

# CMOS Inverter Characterization Report

[Your Name] Roll No: 230616 Technology: 45nm CMOS VDD: 1.8V

July 3, 2025

## 1 Objective

To design and characterize a CMOS inverter using Cadence Virtuoso. The project includes analysis of voltage transfer characteristics (VTC), noise margins, propagation delays, rise/fall times, and dynamic power.

## 2 Technology and Simulation Details

The CMOS inverter is designed using the Cadence Virtuoso environment with 45nm technology node. The following setup was used:

- **PDK Used:** GPDK045v5
- **Library:** analogLib
- **Simulation Tool:** ADE L
- **Waveform Viewer:** ViVA
- **Supply Voltage (VDD):** 1.8V

### Transistor Parameters

Device	Width (W)	Length (L)
NMOS	0.265 $\mu\text{m}$	0.045 $\mu\text{m}$
PMOS	0.385 $\mu\text{m}$	0.045 $\mu\text{m}$

Table 1: MOSFET Dimensions

# 3 Schematic and Simulation Setup

## Inverter Schematic

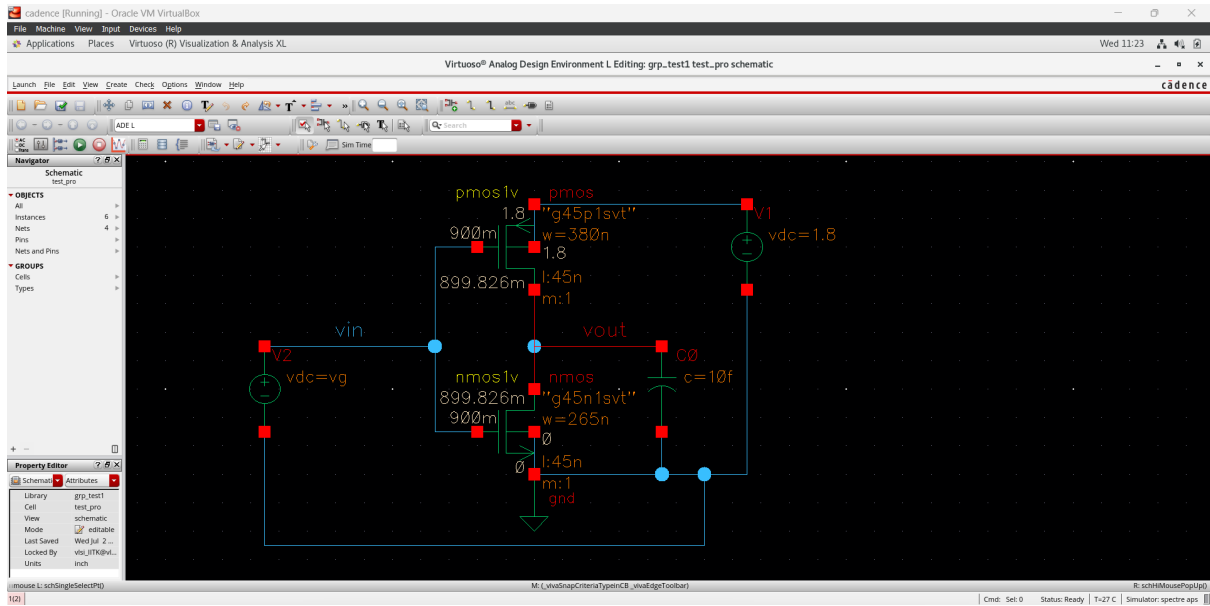


Figure 1: CMOS Inverter Schematic in Virtuoso

## ADE Setup

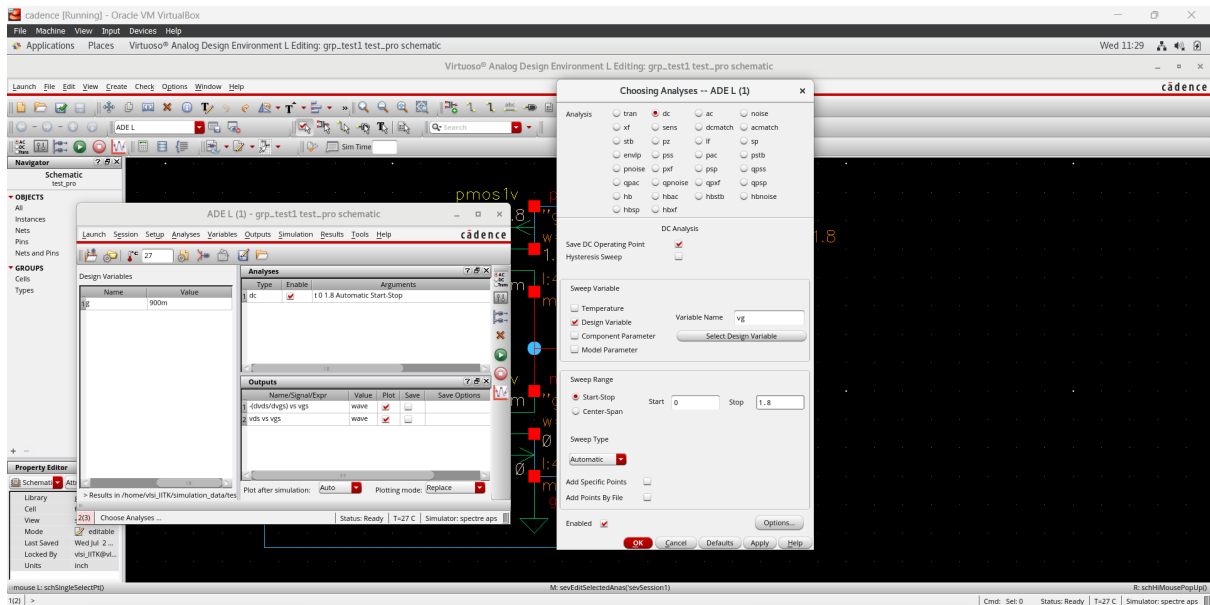


Figure 2: Simulation Setup in ADE

# 4 Voltage Transfer Characteristics (VTC)

## VTC Plot

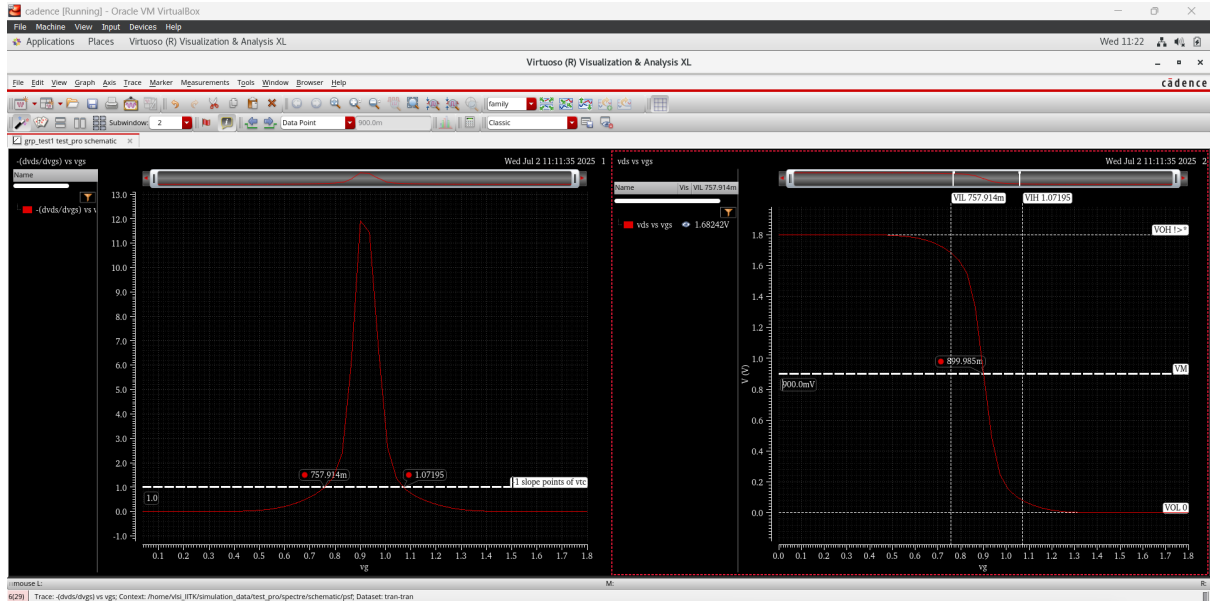


Figure 3: Voltage Transfer Characteristics (VTC)

## Extracted VTC Parameters

Parameter	Value (V)
VOH	1.8
VOL	0.0
VM	0.9
VIL	0.758
VIH	1.072

Table 2: VTC Measurements

## Noise Margins

Margin	Value (V)
Noise Margin High (NMH = VOH - VIH)	0.728
Noise Margin Low (NML = VIL - VOL)	0.758

Table 3: Noise Margin Values

## Simulation Settings

Parameter	Value	Unit
DC Sweep Range	0 to 1.8	V
Pulse Rise Time	50	ps
Pulse Fall Time	50	ps
Pulse Width	1	ns
Pulse Period	2	ns
Total Simulation Time	6	ns
For Power Simulation Time	10	ns

Table 4: Transient and DC Simulation Parameters

## 5 Transient Analysis

### Propagation Delay Measurement

 


Figure 4: Measurement of tpHL and tpLH

Delay Type	Value (ns)
tpHL	0.0379
tpLH	0.0383
Average Delay (tpd)	0.0381

Table 5: Propagation Delays

# Rise and Fall Time

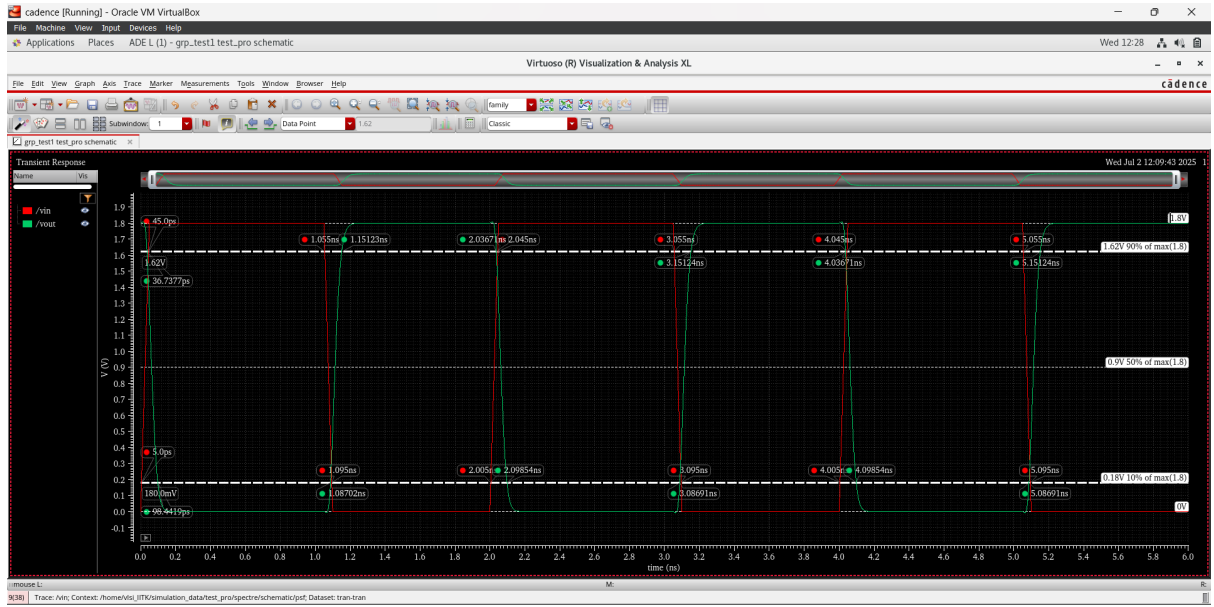


Figure 5: Rise and Fall Time Measurement

Transition	Time (ns)
Rise Time ( $t_r$ )	0.0643
Fall Time ( $t_f$ )	0.0618

Table 6: Rise and Fall Times

## 6 Dynamic Power Analysis

### Instantaneous Power vs Time



Figure 6: Power vs Time Plot

# Average Power

 


Figure 7: Average Power Calculation in ViVA

Parameter	Value
Average Dynamic Power	17.17 $\mu$ W

Table 7: Dynamic Power Result

## 7 Conclusion

The CMOS inverter was successfully designed and simulated using Cadence Virtuoso. All key parameters were extracted and analyzed, including VTC behavior, noise margins, propagation delays, rise/fall times, and power. The results align with theoretical expectations for 45nm CMOS.